
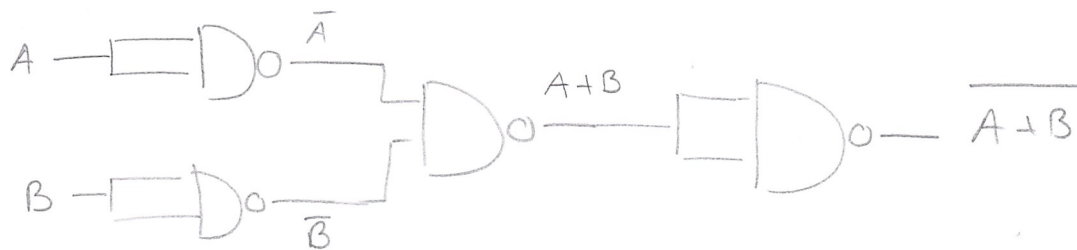


VHDL HW#1


① a) NOR gate with NAND gates
5pts

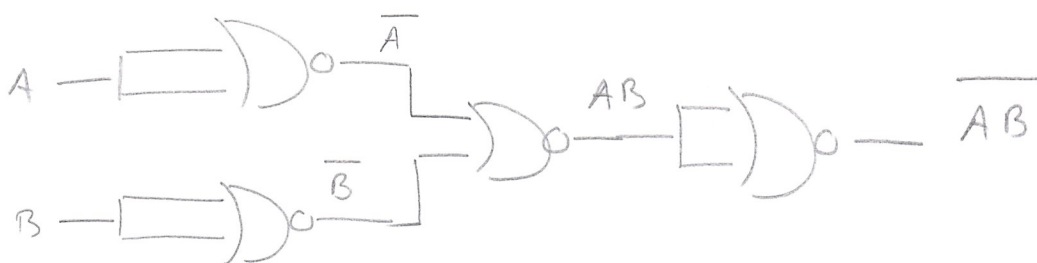

SP15 b) NAND gate with NOR gates




16pts c)

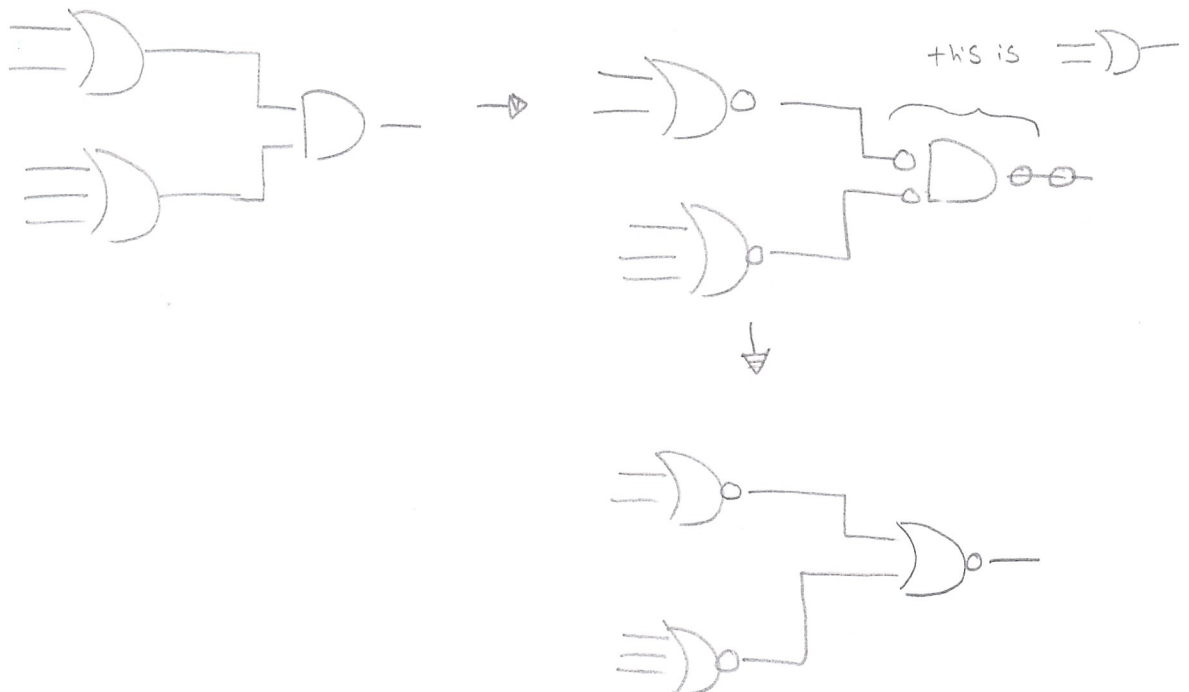


5pts D) it is easier to estimate circuit timings & Power consumption.

2
10pts a)

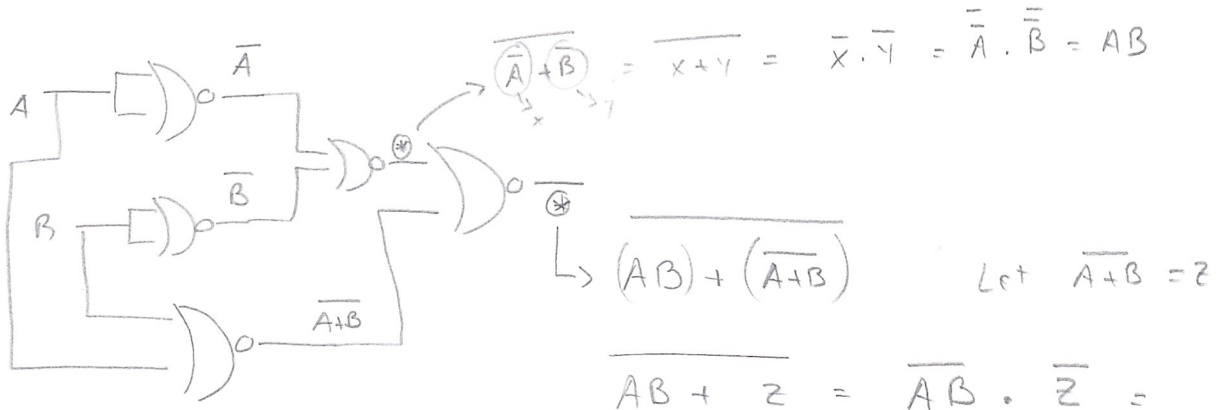

$$(\overline{A+B}) \cdot (\overline{AB}) = (\overline{A+B}) \cdot (A+B) =$$
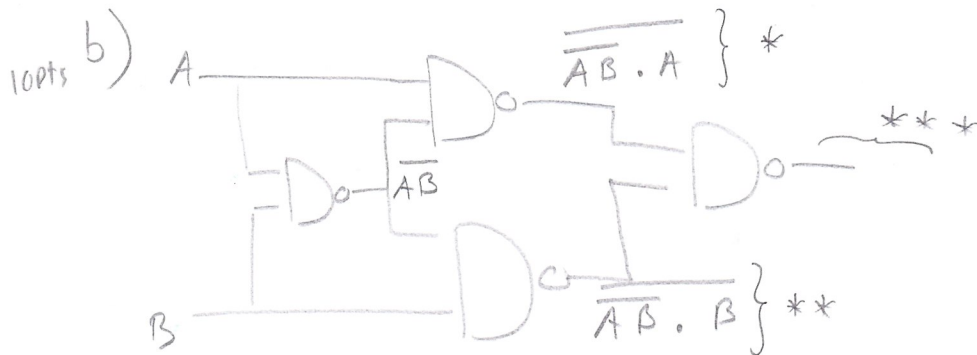
$$\underbrace{\overline{A}A}_{\emptyset} + \overline{A}B + A\overline{B} + \underbrace{\overline{B}B}_{\emptyset} = \overline{A}B + A\overline{B}$$



(*) Let $\overline{AB} = X \Rightarrow \overline{AB} \cdot A = X \cdot A = \overline{X} + A = \overline{\overline{AB}} + A = AB + A$

(**) Let $\overline{AB} = Y \Rightarrow \overline{AB} \cdot B = Y \cdot B = \overline{Y} + B = AB + B$

(***) $(\overline{AB+B}) \cdot (\overline{AB+A}) = (\overline{AB+Z}) \cdot (\overline{AB+W}) = (\overline{AB+Z}) + (\overline{AB+W})$

Let $\overline{B} = Z$
 $\overline{A} = W$

$$= \left[\overline{AB} \cdot \overline{Z} \right] + \left[\overline{AB} \cdot \overline{W} \right] = \left[(\overline{A+B}) \cdot B \right] + \left[(\overline{A+B}) \cdot A \right]$$

$$= \overline{A}B + \overline{B}B + A\overline{B} + A\overline{A} = \overline{A}B + A\overline{B}$$

③ $a + [(b.c).a] = d$


10pts

let $\overline{b.c} = x$


$a + [x.a] = d$

by the absorption law $\rightarrow$


$a = d$

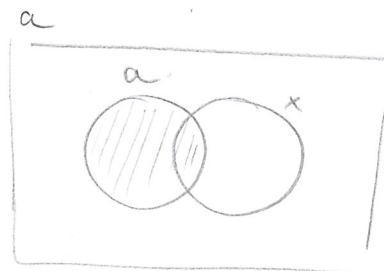


+

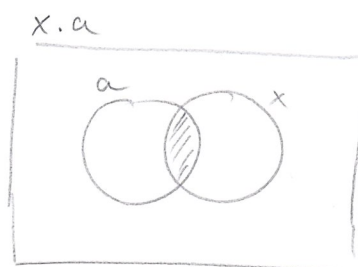

=

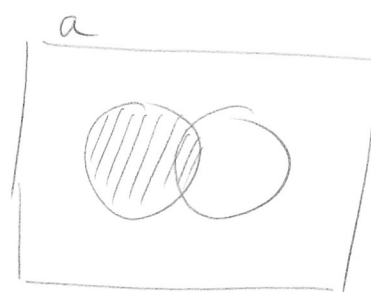


④

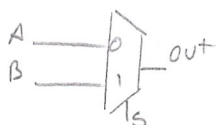

$out = A\bar{B} + BS$


10pts a) Not gate:

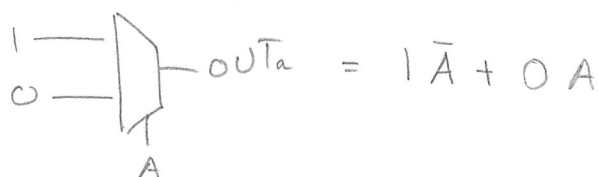


10pts 5) NOR gate with A MUX

Remember
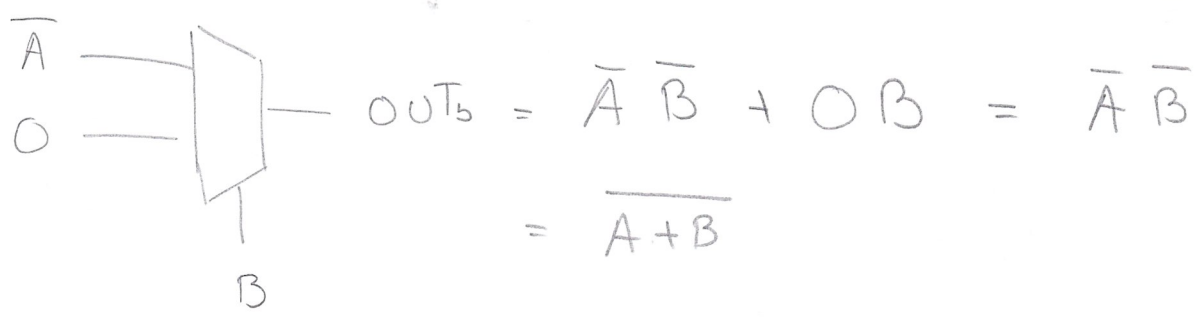
$$\overline{A+B} = \bar{A} \cdot \bar{B}$$





10pts 5

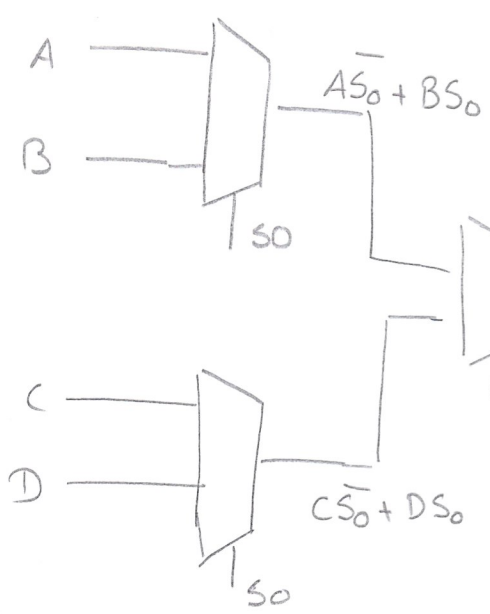

$$OUT = (A\bar{S}_0 + BS_0)\bar{S}_1 + (C\bar{S}_0 + DS_0)S_1$$

$$= A\bar{S}_0\bar{S}_1 + BS_0\bar{S}_1 + C\bar{S}_0S_1 + DS_0S_1$$

5pts 6

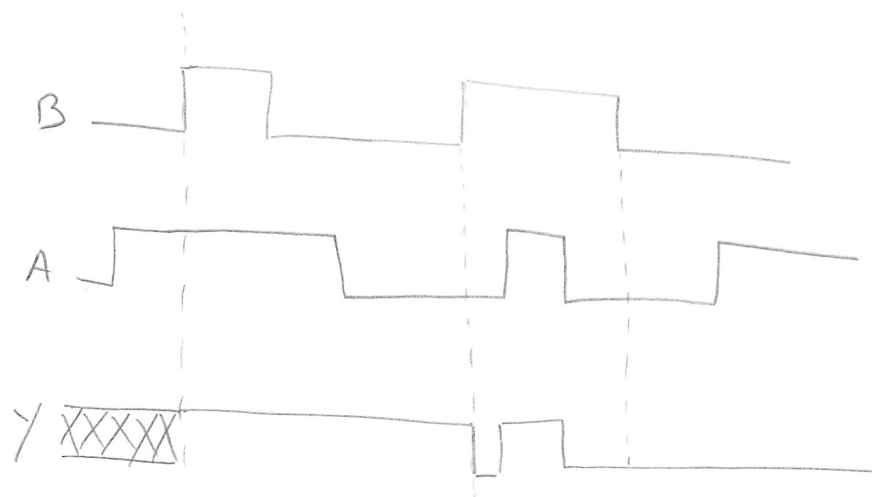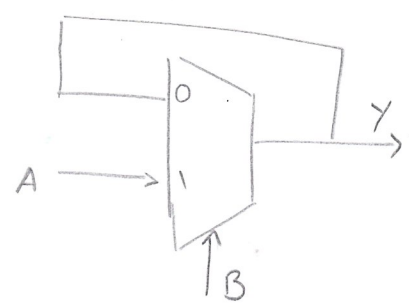

This is A LATCH

- 5pts
- ⑦
- a) 3 clock cycles
 - b) 1 clock cycle
 - c) 3 clock cycles

- 5pts
- ⑧
- IN A FLIP FLOP, THE INPUT IS ONLY PROPAGATED TO AN OUTPUT AT A CLOCK EDGE (EITHER RISING, FALLING or both)
 - IN A LATCH, THE INPUT PROPAGATES TO THE OUTPUT WHENEVER CLOCK IS HIGH